

## Kirchhoff's Rules

### First Rule (Loop Rule)

The change in potential around a closed loop is always equal to zero.

### Second Rule (Junction Rule)

The sum of the currents entering a junction must equal the sum of the currents leaving a junction.

Conventions When Tracing a Loop:


1. Resistors:

- If you go across a resistor in the **same direction** as the current, the potential **decreases** by  $I \cdot R$ .
- If you go across a resistor in the **opposite direction** as the current, the potential **increases** by  $I \cdot R$ .

2. Batteries:


- If you encounter the **positive** side of the battery first, the potential **decreases** by the battery's voltage.
- If you encounter the **negative** side of the battery first, the potential **increases** by the battery's voltage.

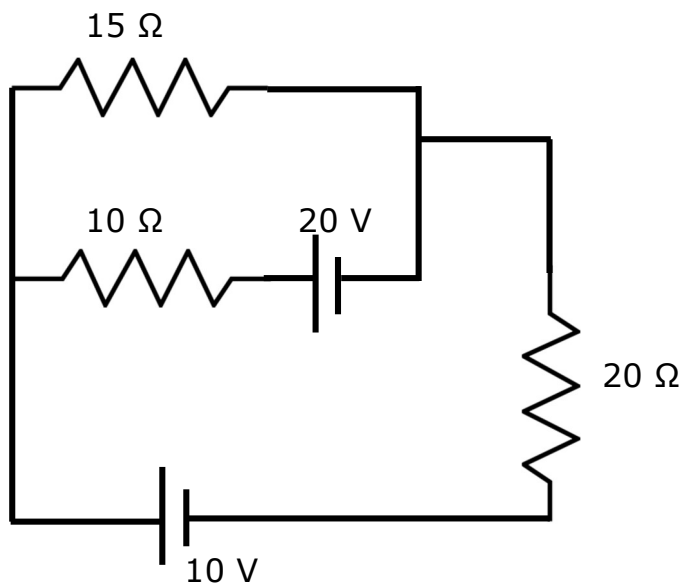Example: Determine the current that flows through each resistor.




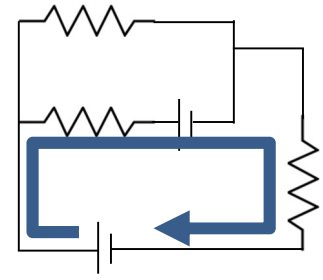1. Use the First Rule around both loops.

Lower loop:  $10 \text{ V} - I_2 (10 \Omega) - 20 \text{ V} - I_1 (20 \Omega) = 0$



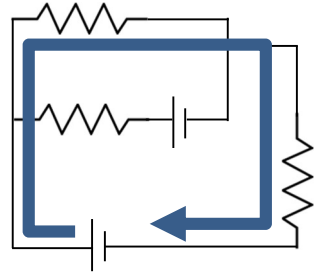Upper loop:  $10 \text{ V} - I_3 (15 \Omega) - I_1 (20 \Omega) = 0$



2. The sum of the currents on the two branches equals the total current.

$$I_1 = I_2 + I_3$$

3. Rearrange the equations get the Is and numbers in columns.

$$\begin{array}{rrcr} -I_1 (20 \Omega) - I_2 (10 \Omega) + I_3 (0) & = & 10 \text{ V} \\ -I_1 (20 \Omega) - I_2 (0) & - & I_3 (15 \Omega) & = -10 \text{ V} \\ I_1 & & -I_2 & -I_3 = 0 \end{array}$$

4. Enter the equations into matrices and solve.

$$[A] = \begin{bmatrix} -20 & -10 & 0 \\ -20 & 0 & -15 \\ 1 & -1 & -1 \end{bmatrix} \quad [B] = \begin{bmatrix} -10 \\ -10 \\ 0 \end{bmatrix}$$

Solution:

$$I_1 = -0.0769 \text{ A}$$

$$I_2 = -0.8462 \text{ A}$$

$$I_3 = 0.7692$$

Currents 1 and 2 are negative which means the current goes in the opposite direction than the one initially chosen.